

AC Overview

I. Components

- Capacitors (C) [Section 6.2, 6.3]
- Inductors (L) [Section 6.4, 6.5]
- C & L vs. R $\rightarrow$ Storage vs. Dissipation [Section 6.1]

Alexander & Sadiku,
“Fundamentals of Electric Circuits”
5th Edition Chapters 6, 9

II. Concepts


- Sinusoids [Section 9.1, 9.2]
- Phasors (complex numbers) [Section 9.3, 9.4]
- Impedance & Admittance [Section 9.5]

III. Combine and apply

- Apply Kirchhoff's laws in Frequency Domain [Section 9.6]
- Impedance combinations [Section 9.7]

AC (Alternating Current):




Usual waveform is sinusoidal wave

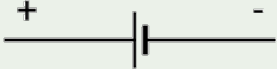	Direct Current	Alternating Current
Abbreviation	DC	AC
Electrode	Fixed positive, negative electrodes	“Alternating” positive, negative electrodes
Current Direction	Current always flowing out of the positive pole	Reverse direction periodically
Circuit Symbol		
Common Power Supply	Battery	Household Power

Capacitor and Capacitance

Capacitor

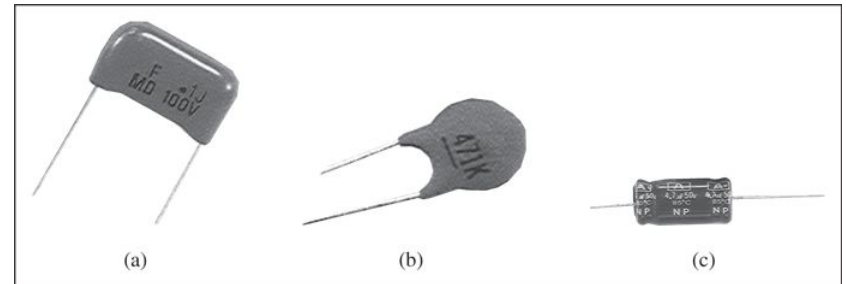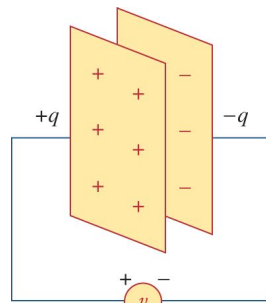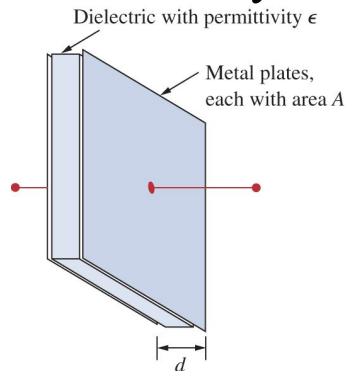- Simplest way to form a capacitor is to sandwich an insulator (technical term is dielectric) between a pair of parallel conducting plates
- Hence the symbol for a capacitor is two parallel lines separated by a gap



$$Q = CV$$

A circuit symbol for a capacitor, consisting of two parallel vertical lines. Above the symbol is the letter 'C'. Below the symbol is a voltage source v with '+' and '-' signs.

Capacitance

- Commonly symbolized by the letter C with unit of Farads (F)
- Relates the amount of charge stored for a given voltage applied
- No energy dissipated unlike resistors
- Energy is stored (in keeping the plates apart)

DC and AC response in Capacitor

$$\begin{array}{c} + \\ V \\ - \end{array} \begin{array}{c} \text{---} \\ \text{---} \\ \text{---} \end{array} \begin{array}{c} \circ \\ \text{---} \\ \circ \end{array} \quad Q(t) = CV(t) \xrightarrow[\text{with respect to time}]{\text{Differentiate}} \boxed{i(t) = C \frac{dV(t)}{dt}}$$

If voltage is constant with time: $dV/dt = 0 \rightarrow I = 0$

No voltage change $\rightarrow$ No current

Case study to consider:

Given that $C = 1 \text{ nF}$

If $V(t) = 1 \sin(10t) \rightarrow Q(t) = \underline{\hspace{4cm}}$

$\rightarrow i(t) = \underline{\hspace{4cm}}$

If voltage changes with time: $dV/dt \neq 0 \rightarrow I \neq 0$

Voltage change $\rightarrow$ Charge changes $\rightarrow$ Current

Summary: Capacitor response to DC & AC

1) If applied voltage is DC

- Insulating dielectric blocks the current from flowing through
- Plates will charge up
- At DC, capacitor blocks current from flowing through




2) If applied voltage is AC (e.g. sine wave)

- Charge on the plates also likewise varies in time with the AC
- Capacitor therefore does not act as an open circuit in the presence of an AC
- In AC, capacitor allows current to pass through


Inductors and Inductance

Inductor

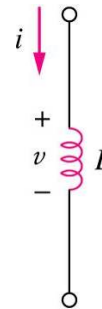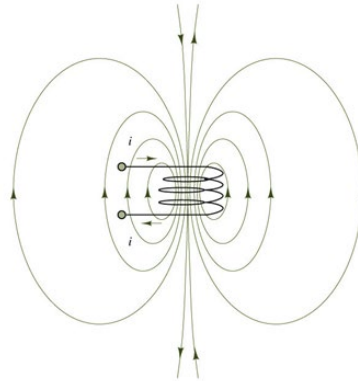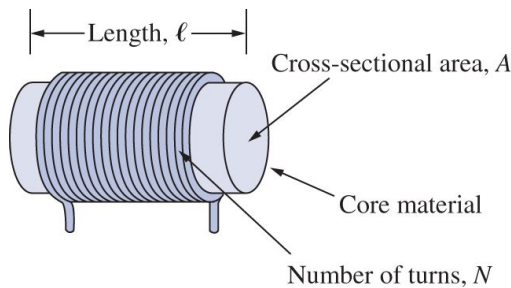- Simplest way to form an inductor is to winding a coil around a core that concentrates magnetic field lines (flux)
- Hence symbol of an inductor is coil between two terminals



$$\phi = Li$$

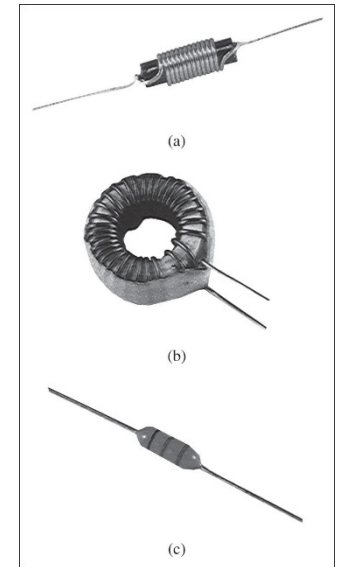


Inductance

- Inductance is commonly symbolized by letter L with unit of Henrys (H)
- Passing a current through an inductor produces a magnetic flux (ϕ) that is related to the inductance (L)
- No energy dissipated unlike resistors (note that wires are assumed to have no resistance by definition)

I-V relation in an inductor

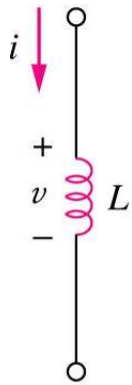If the current through an inductor is time-varying, then the generated voltage must also be time-varying:



$$\text{Flux: } \phi = Li$$

$$\text{Faraday's Law: } v(t) = \frac{d\phi(t)}{dt}$$

$$\text{Differentiating with respect to time (t): } v(t) = L \frac{di(t)}{dt}$$

Voltage depends on the rate of change of current

If current is constant with time $\rightarrow di/dt = 0 \rightarrow V = 0$ (No voltage)

No current change $\rightarrow$ No voltage difference

If current changes with time $\rightarrow di/dt \neq 0 \rightarrow V \neq 0$ (There is voltage)

Current change $\rightarrow$ Voltage difference

Sinusoids

Sinusoids can be written as sine or cosine functions

$$x(t) = A \sin(\omega t + \phi)$$

A = amplitude

ω = radian frequency = $2\pi f$ (rad/s)

f = natural frequency (cycles/s or Hz)


T = period = $1/f$ (second)

ϕ = phase (with reference to a cycle: 2π)


We compare the two waves by:

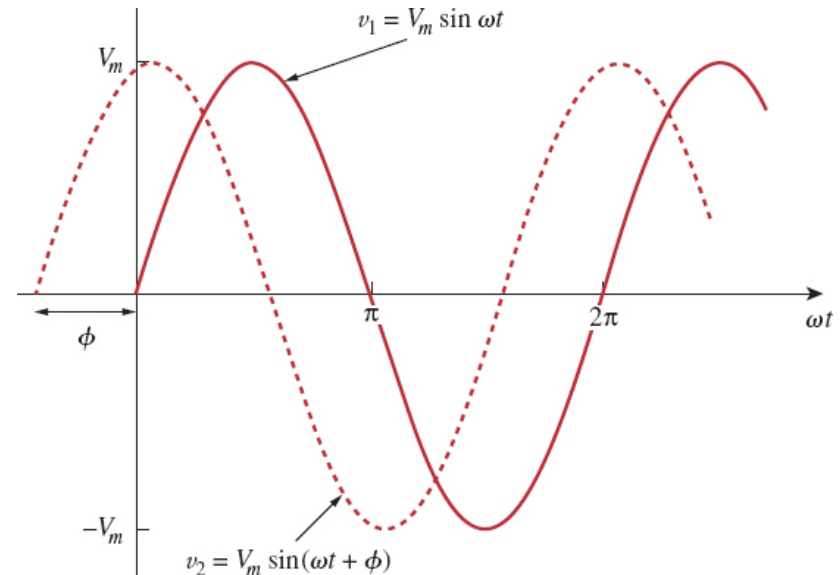- 1) The ratio of their amplitudes
- 2) Phase difference

We can immediately see that an AC signal has as lot more key features than a DC signal. For a DC signal, the magnitude alone is a sufficient quantitative description. But in the case of sinusoidal AC signals, concepts like frequency and phase also need to be considered.



I-V relationship in a resistor

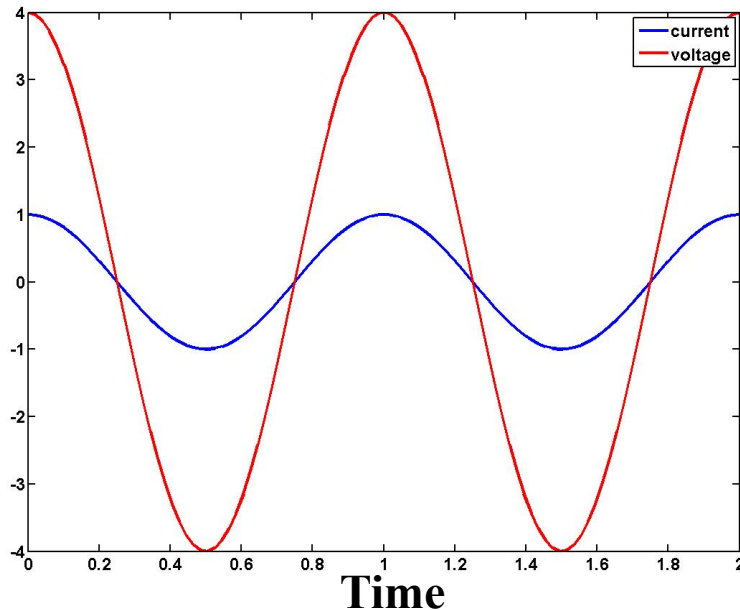


This plot shows the relationship between the current and voltage in a 4Ω resistor when the signal is an AC sinusoid.

It can be seen that there is no phase difference between the voltage and current.

This is because R is simply given by the ratio of voltage to current and there is therefore no phase shift between the two, but simply a scaling in the amplitude.

I-V relationship in a capacitor

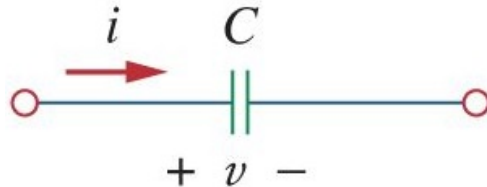

If the voltage across a capacitor is: $V(t) = V_m \cos(\omega t)$

Then the current through it will be:

$$I(t) = C(dV/dt) = -\omega C V_m \sin(\omega t) = \omega C V_m \cos(\omega t + 90^\circ)$$


Shift forward by 90°

Therefore we say that I leads V by 90°

(or $\pi/2$ in radians)


$$\frac{V_m}{I_m} = \frac{1}{\omega C}$$

$$\angle V - \angle I = -\frac{\pi}{2}$$

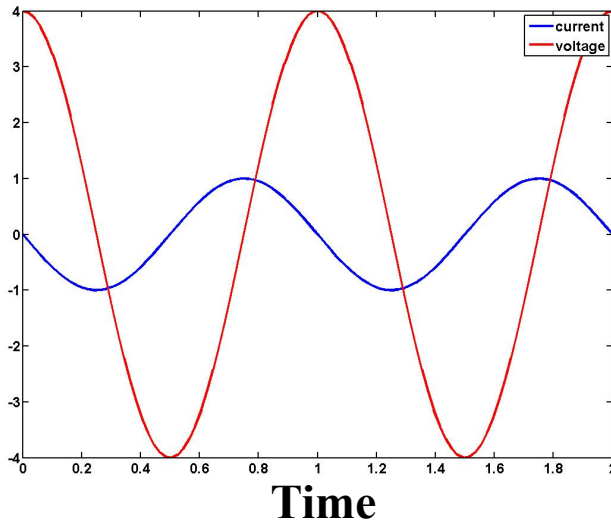

- 1) Current goes through a phase shift relative to the voltage (in a resistor, there is no phase shift between the current and voltage)
- 2) Ratio of voltage to current depends on the capacitance **AND** frequency of the sinusoid (in a resistor, the ratio between voltage and current is simply R and independent of frequency)


I-V relationship in an inductor

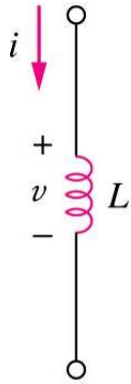

If the current through an inductor is: $i(t) = I_m \cos(\omega t)$

Then the current through it will be:
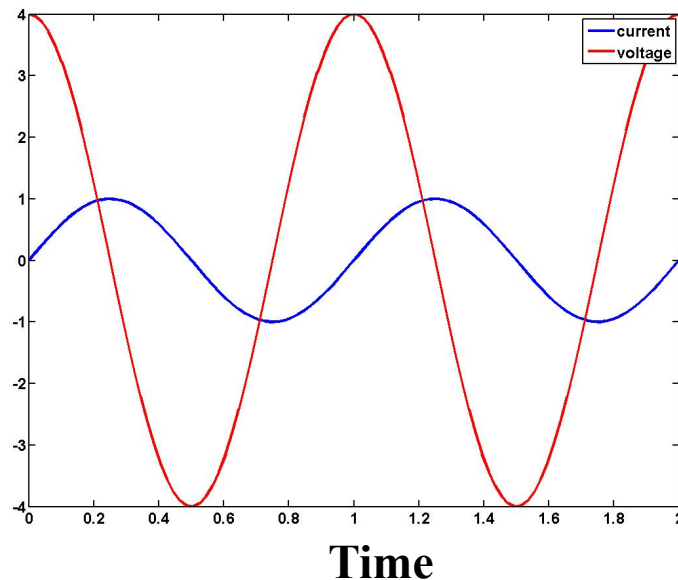
$$v(t) = L(di/dt) = -\omega L I_m \sin(\omega t) = \omega L I_m \cos(\omega t + 90^\circ)$$



Shift forward by 90°

Therefore we say that I lags V by 90°
(or $\pi/2$ in radians)


$$\frac{V_m}{I_m} = \omega L \quad \angle V - \angle I = +\frac{\pi}{2}$$

- 1) Current goes through a phase shift relative to the voltage
- 2) Ratio of voltage to current depends on inductance AND frequency of the sinusoid

Graphical methods


Calculate the phase angle between:
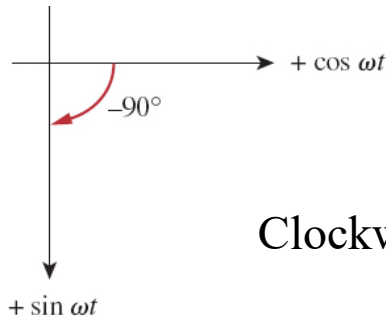
$$v_1 = -10 \cos(\omega t + 50^\circ) \text{ and } v_2 = 12 \sin(\omega t - 10^\circ)$$



(a)


Clockwise: Phase goes backward (-ve)

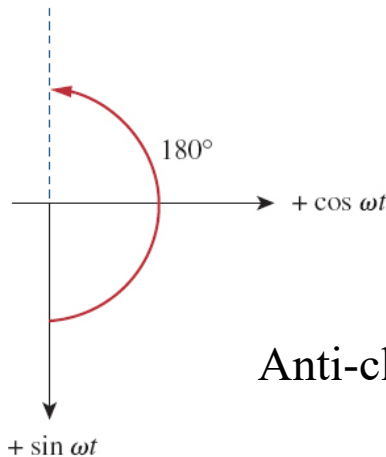

(b)


Anti-clockwise: Phase goes forward (+ve)

$$\angle v_1 - \angle v_2 = -30^\circ$$

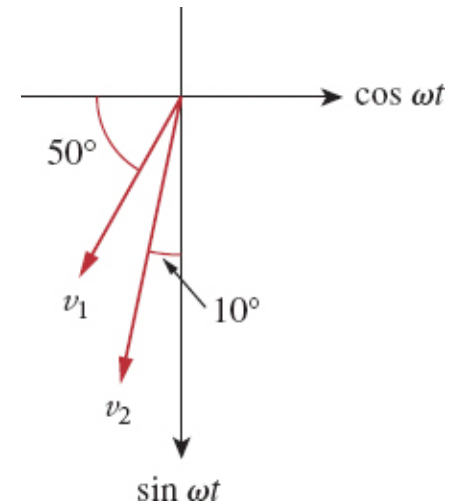

Phasors

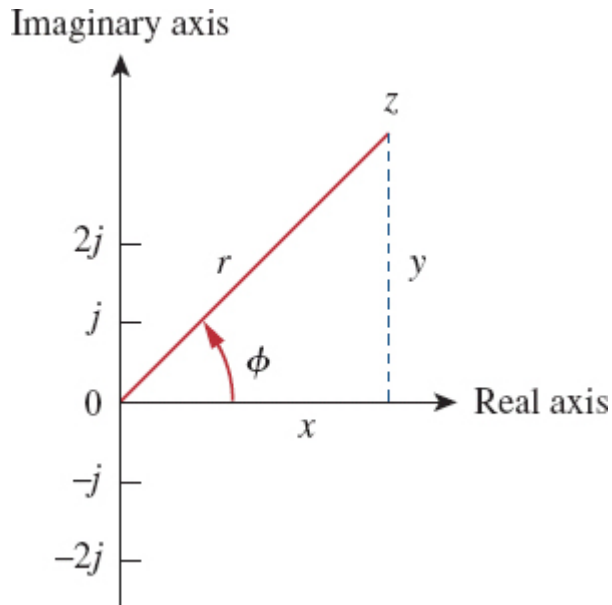- A phasor is a complex number that represents the amplitude and phase of a sinusoid
- Phasors are more convenient to work with than sine and cosine functions and are a powerful tool for analyzing circuits



A complex number z can be expressed in **rectangular/cartesian form** as:

$$z = x + jy$$

Imaginary unit: $j = \sqrt{-1}$

x : real part $\rightarrow \text{Re}(z) = x$; y : imaginary part $\rightarrow \text{Im}(z) = y$

The complex number z can be expressed in **polar form** or **exponential form** as:

$$z = r \angle \phi = r e^{j\phi}$$

$$r = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1} \frac{y}{x}$$

$$x = r \cos \phi \quad y = r \sin \phi$$

Euler's identity

$$e^{+j\phi} = \cos \phi + j \sin \phi$$

Review : Complex Numbers

$$3 + 4j = 5\angle 53^\circ = 5e^{j(53^\circ)}$$

$$3 - 4j = 5\angle (-53)^\circ = 5e^{j(-53^\circ)}$$

$$1 + j = \sqrt{2}\angle 45^\circ = \sqrt{2}e^{j(45^\circ)}$$

$$1 - j = \sqrt{2}\angle (-45)^\circ = \sqrt{2}e^{j(-45^\circ)}$$

$$6 + 6\sqrt{3}j = 12\angle 60^\circ = 12e^{j(60^\circ)}$$

$$6 - j6\sqrt{3}j = 12\angle (-60)^\circ = 12e^{j(-60^\circ)}$$

Complex number arithmetic

The following mathematical operations are important.

Addition

$$z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

Subtraction

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication

$$z_1 z_2 = r_1 r_2 \angle (\phi_1 + \phi_2)$$

Division

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle (\phi_1 - \phi_2)$$

Reciprocal

$$\frac{1}{z} = \frac{1}{r} \angle (-\phi)$$

Square Root

$$\sqrt{z} = \sqrt{r} \angle (\phi/2)$$

Complex Conjugate

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

Phasors

A phasor represents a sinusoid as the real component of a vector in the complex plane representation based on Euler's identity:

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

$$\cos \phi = \operatorname{Re}(e^{j\phi}) \quad \sin \phi = \operatorname{Im}(e^{j\phi})$$

Given a sinusoid: $v(t) = V_m \cos(\omega t + \phi)$


$$v(t) = \operatorname{Re}(V_m e^{j(\omega t + \phi)}) = \operatorname{Re}(V_m e^{j\omega t} e^{j\phi})$$

$$v(t) = \operatorname{Re}(V_m e^{j\phi} e^{j\omega t}) = \operatorname{Re}(V e^{j\omega t})$$

, where $V = V_m e^{j\phi} = V_m \angle \phi$

The **length** of the vector is the **amplitude** of the sinusoid.

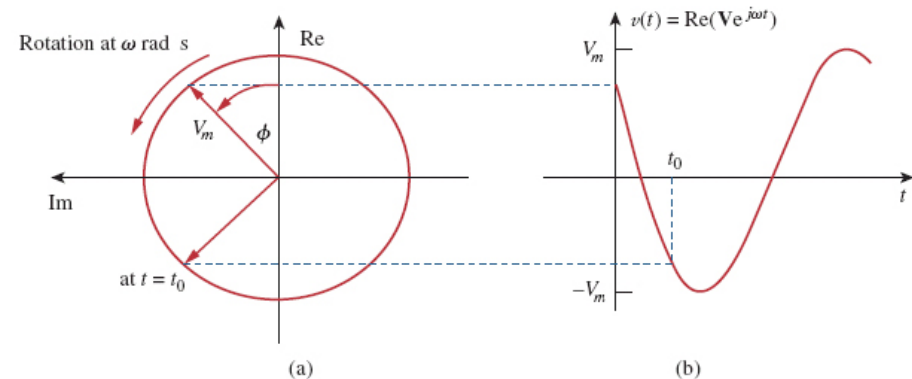The **angle** ϕ of the vector with respect to the positive real axis is the **phase**.



$v(t) = V_m \cos(\omega t + \phi)$	$\Leftrightarrow$	$V = V_m \angle \phi$
(Time-domain representation)		(Phasor-domain representation)

Sinusoid-Phasor Transformation

NOTE:

- When the sinusoid is expressed as a phasor, the time factor, $e^{j\omega t}$, is suppressed.
- When using phasors, always keep in mind that it is of a single frequency ω only.

Sinusoid to phasor:

- (i) express the sinusoid in the cosine form,
- (ii) write it as the real part of a complex number,
- (iii) “suppress” the time factor $e^{j\omega t}$

Phasor to sinusoid:

$$v(t) = \text{Re}(\mathbf{V} e^{j\omega t})$$

TABLE 9.1

Sinusoid-phasor transformation.

Time domain representation	Phasor domain representation
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	$I_m \angle \theta$
$I_m \sin(\omega t + \theta)$	$I_m \angle \theta - 90^\circ$

Why Phasor? Arithmetic in Superposition

- It is easier to carry out the superposition of sine waves using phasor than adding sine functions directly in the time domain.
- Example: Calculate the sum of the following three sinusoidal signals directly:

$$v_1(t) = 2\sqrt{3} \cos\left(\omega t + \frac{\pi}{6}\right)$$

$$v_2(t) = 6 \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$v_3(t) = 2\sqrt{3} \sin\left(\omega t + \frac{\pi}{3}\right)$$


Example (Arithmetic in Superposition)

Calculate $v_1(t) + v_2(t) + v_3(t)$:

$$v_1(t) = 2\sqrt{3} \cos\left(\omega t + \frac{\pi}{6}\right)$$

$$v_2(t) = 6 \cos\left(\omega t - \frac{\pi}{2}\right)$$
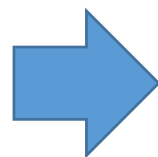
$$v_3(t) = 2\sqrt{3} \sin\left(\omega t + \frac{\pi}{3}\right)$$



Convert to phasor:

$$V_1 = 2\sqrt{3} \angle \frac{\pi}{6}$$

$$V_2 = 6 \angle -\frac{\pi}{2}$$

$$V_3 = 2\sqrt{3} \angle -\frac{\pi}{6}$$

$$V_1 + V_2 + V_3 = 3 + \sqrt{3}j - 6j + 3 - \sqrt{3}j = 6 - 6j = 6\sqrt{2} \angle -\frac{\pi}{4}$$

$$v_1(t) + v_2(t) + v_3(t) = 6\sqrt{2} \cos\left(\omega t - \frac{\pi}{4}\right)$$

Sinusoid-phase transformation

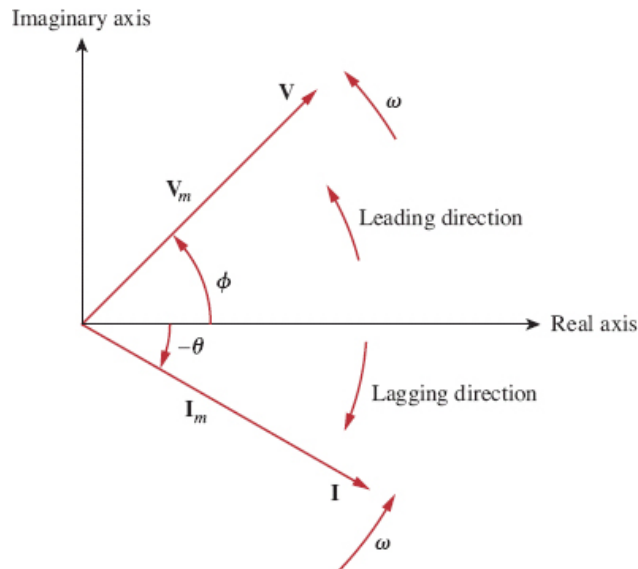


TABLE 9.1

Sinusoid-phasor transformation.


Time domain representation	Phasor domain representation
$V_m \cos(\omega t + \phi)$	$V_m \angle \phi$
$V_m \sin(\omega t + \phi)$	$V_m \angle \phi - 90^\circ$
$I_m \cos(\omega t + \theta)$	$I_m \angle \theta$
$I_m \sin(\omega t + \theta)$	$I_m \angle \theta - 90^\circ$

$v(t)$	V
Time-domain function (also called instantaneous time representation)	Frequency domain (also called phasor domain representation).
Time-dependent	NOT time dependent ($e^{j\omega t}$ already suppressed)
Always real	Generally complex

Phasor analysis is valid only when the frequency is constant!

The meaning of “j”

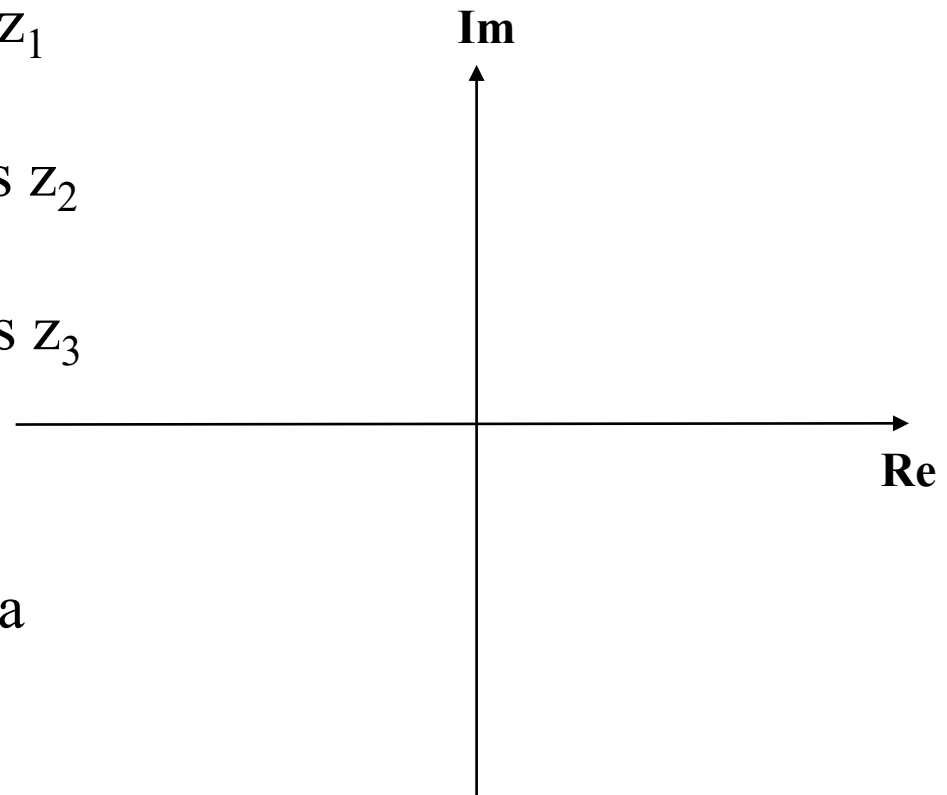- 1) Draw $z = 3$ on the Im-Re graph
- 2) Multiply z by j , name this as z_1 and draw it on the graph
- 3) Multiply z by $-j$, name this as z_2 and draw it on the graph
- 4) Multiply z by -1 , name this as z_3 and draw it on the graph



What is the effect of multiplying a number by j , $-j$, or -1 ?

Why Phasor? (Differentiation and Integration)

Differentiation and integration of a sinusoidal time-domain function will become a simple algebraic multiplication or division in the phasor domain:

Derivative:



$$\frac{dv}{dt} \Leftrightarrow j\omega V$$

Integral:

$$\int v dt \Leftrightarrow \frac{V}{j\omega}$$



Phasor Relationships for Resistors

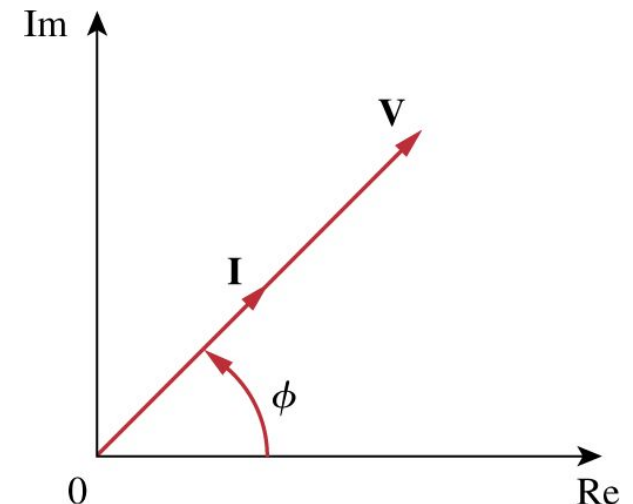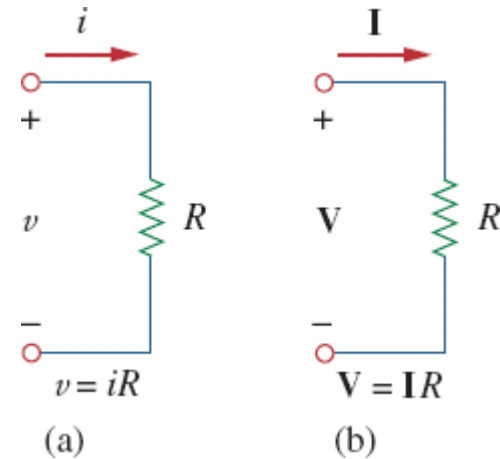- 1) Each circuit element has a relationship between its current and voltage.
- 2) These can be mapped into phasor relationships very simply for resistors capacitors and inductor.
- 3) For the resistor, the voltage and current are related via Ohm's law.
- 4) As such, the voltage and current are in phase with each other.





Phasor Relationships for Inductors

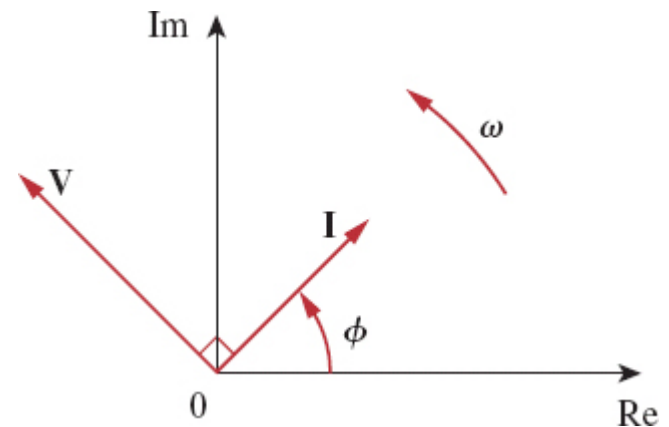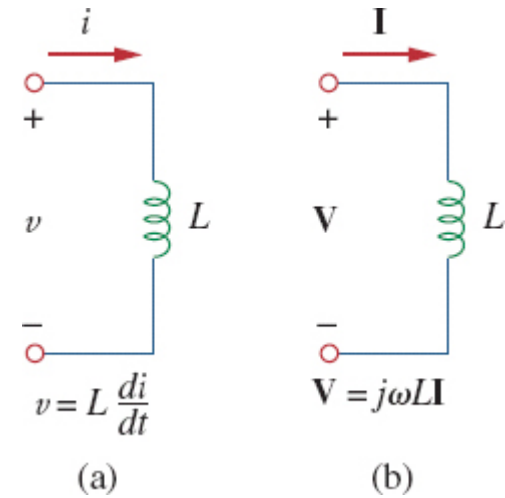- 1) Inductors on the other hand have a phase shift between the voltage and current.
- 2) In this case, the voltage leads the current by 90° .
- 3) Or one says the current lags the voltage, which is the standard convention.
- 4) This is represented on the phasor diagram by a positive phase angle between the voltage and current.



Phasor Relationships for Capacitors

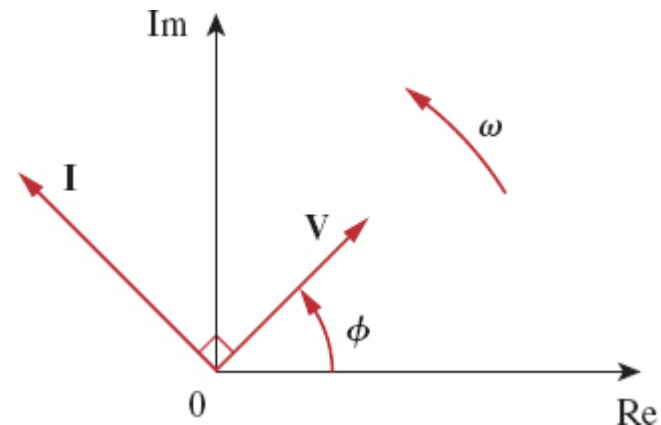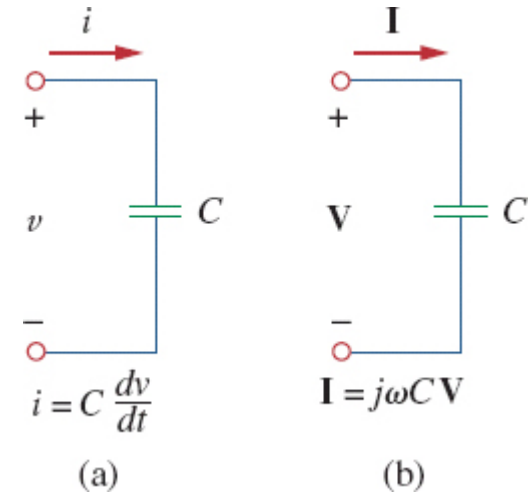- 1) Capacitors have the opposite phase relationship as compared to inductors.
- 2) In their case, the current leads the voltage.
- 3) In a phasor diagram, this corresponds to a negative phase angle between the voltage and current.



Why Phasor? (Differentiation and Integration)

With phasors, we can observe Ohm's Law for inductors and capacitors as found for resistors, rather than solving differential equations in AC circuits.

TABLE 9.2

Summary of voltage-current relationships.

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Voltage current relationships

TABLE 9.2

Summary of voltage-current relationships.

Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Impedance and Admittance

We can now expand Ohm's law to capacitors and inductors. This would have been otherwise tricky as the ratios of voltage and current always changing when working in the time-domain form. In frequency domain it is straightforward.

The impedance of a circuit element is the ratio of the phasor voltage to the phasor current, commonly represented by Z .

$$Z = \frac{V}{I} \quad \text{or} \quad V = ZI \quad \text{Admittance is simply the inverse of impedance: } Y = 1/Z$$

Impedance and Admittance

- In the frequency domain, the values obtained for impedance are only valid at that frequency.
- Changing to a new frequency will require recalculating the values.
- The impedance of capacitors and inductors are shown here:

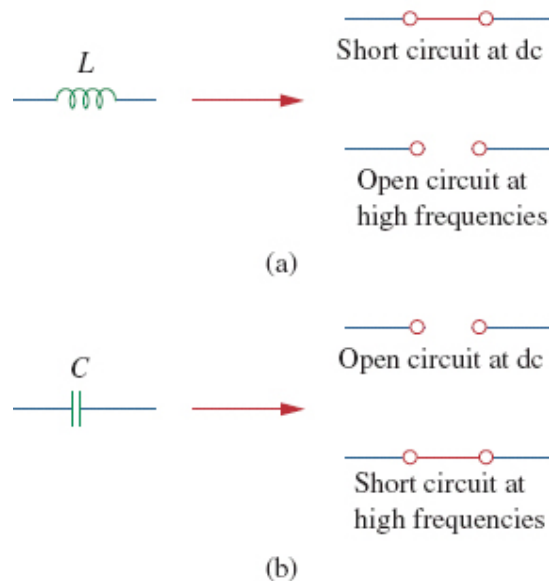


TABLE 9.3


Impedances and admittances of passive elements.

Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

Applying Kirchhoff's in frequency domain

Phasors allow Kirchhoff's laws to be applicable. Therefore a circuit transformed to the frequency domain can be evaluated by the same methods developed for KVL and KCL.

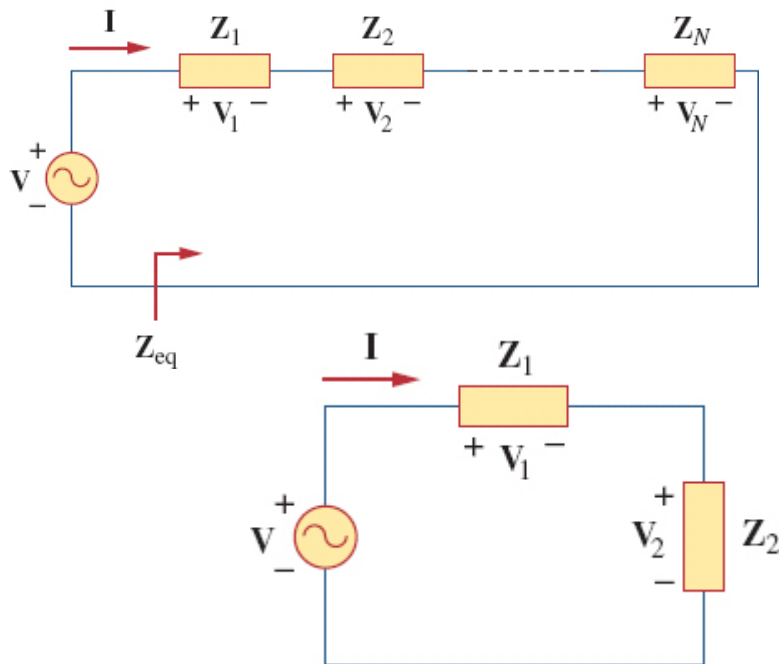Once in the frequency domain, the impedance elements can be combined using the rules for resistors.



Series combinations will result in a sum of the impedance elements:

$$Z_{eq} = Z_1 + Z_2 + Z_3 + \dots + Z_N$$


Elements in series can act like a voltage divider:

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

Parallel combination

Elements combined in parallel will combine in the same fashion as resistors in parallel:
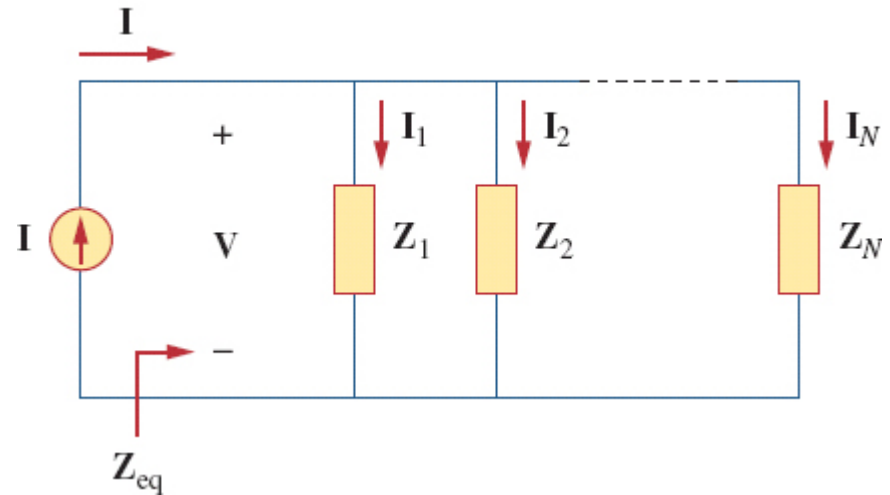
$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \cdots + \frac{1}{Z_N}$$



Expressed as admittance, they are again a sum:

$$Y_{eq} = Y_1 + Y_2 + Y_3 + \cdots + Y_N$$


Impedance: Example 1

Problem 4.61

Work out the impedance (Z) seen across the terminals

When (i) $\omega = 4$ rad/s, (ii) $\omega = 8$ rad/s

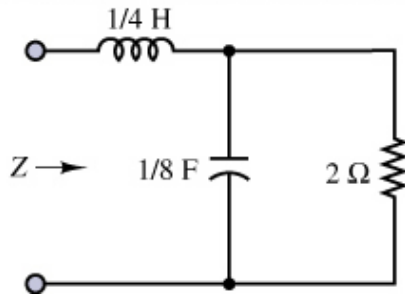Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(i) At 4 rad/s:

Impedance of L:

$$X_L = j\omega L = j(4)(1/4) = j$$

Impedance of C:

$$X_C = 1/j\omega C = 1/[j(4)(1/8)] = -j2$$

Impedance: Example 1 (i) 4 rad/s

When $\omega = 4 \text{ rad/s}$: $X_L = j\omega L = j$; $X_C = 1/j\omega C = -j2$

Impedance of C and parallel with R:

$$\begin{aligned} Z_{RC} &= \frac{X_C R}{R + X_C} = \frac{(-j2)(2)}{2 - j2} = -\frac{j2(1 + j)}{(1 - j)(1 + j)} = -\frac{j2(1 + j)}{2} \\ &= 1 - j \end{aligned}$$

Z_{RC} is in series with impedance of L: $Z = Z_{RC} + X_L$

$$\begin{aligned} &= 1 - j + j \\ &= 1\Omega \end{aligned}$$

Impedance: Example 1 (ii) 8 rad/s

When $\omega = 8 \text{ rad/s}$:

$$X_L = j\omega L = j(8)(1/4) = j2;$$

$$X_C = 1/j\omega C = -j/[(8)(1/8)] = -j$$

Impedance of C and parallel with R: $Z_{RC} = \frac{X_C R}{R + X_C} = \frac{(-j)(2)}{2 - j}$

$$= \frac{-j2(2 + j)}{(2 - j)(2 + j)} = \frac{2}{5}(1 - j2)$$

Z_{RC} is in series with impedance of L: $Z = Z_{RC} + X_L$

$$= \frac{2}{5}(1 - j2) + j2$$
$$= 0.4 + j1.2$$


Impedance depends on the frequency

Impedance: Example 2

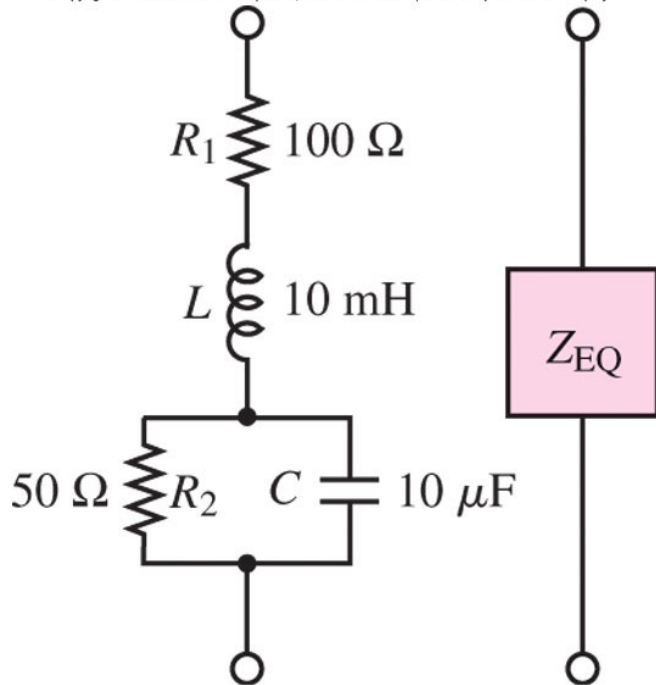Example 4.14 of Rizzoni

Find the equivalent impedance (Z_{EQ}) and admittance (Y_{EQ}) seen across the terminals

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Impedance of L:

$$X_L = j\omega L = j(10^4)(10^{-2}) = j100$$

Impedance of C:

$$X_C = 1/j\omega C = 1/[j(10^4)(10^{-5})] = -j10$$

Given: $\omega = 10^4\text{ rad/s}$

Impedance: Example 2 Solution

Impedance of C parallel R_2 :

$$\begin{aligned}Z_{RC} &= \frac{X_C R}{R + X_C} \\&= \frac{(-j10)(50)}{50 - j10} \\&= \frac{500}{10 + j50} \\&= \frac{50}{1 + j5}\end{aligned}$$

Impedance of L series R_1 :

$$\begin{aligned}Z_{RL} &= X_L + R \\&= 100 + j100 \\&= 100(1 + j)\end{aligned}$$

$$\begin{aligned}Z_{EQ} &= Z_{RC} + Z_{RL} \\&= \frac{50}{1 + j5} + 100(1 + j) \\&= 101.92 + j90.385 \\&= 136.2 \angle 41.57^\circ \Omega\end{aligned}$$

$$\begin{aligned}Y_{EQ} &= 1/Z_{EQ} = (1/136.2) \angle -41.6^\circ S \\&= 7.342 \angle -41.6^\circ mS\end{aligned}$$

Admittance

Admittance is simply the **inverse** of the **impedance**: $Y = 1/Z$

Admittance likewise comprises both real and imaginary parts

$$Y = \mathbf{G} + \mathbf{jB}$$

Real part is called the **AC conductance**

Imaginary part is called the **susceptance**

$$\begin{aligned} Y &= \frac{1}{Z} = \frac{1}{R + jX} = \frac{1}{R + jX} \left(\frac{R - jX}{R - jX} \right) \\ &= \frac{R - jX}{R^2 + X^2} \end{aligned}$$

$$G = \frac{R}{R^2 + X^2}$$

$$B = -\frac{X}{R^2 + X^2}$$

Example on Admittance



$$Z_{ab} = R_1 + j\omega L$$

$$Y_{ab} = 1/Z_{ab} = 1/(R_1 + j\omega L)$$

$$Y_{ab} = \frac{R_1}{R_1^2 + (\omega L)^2} - \frac{j\omega L}{R_1^2 + (\omega L)^2}$$

$$Y_{ab} = 1/Z_{ab} = 1/R_2 + j\omega C$$

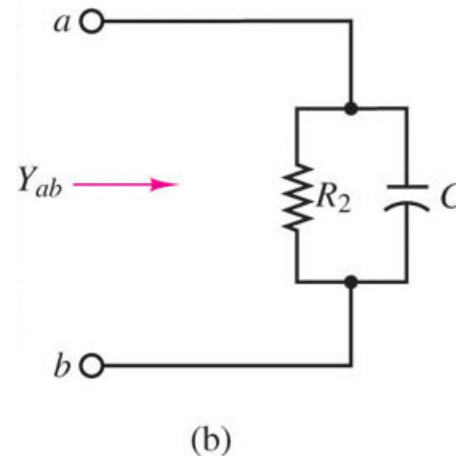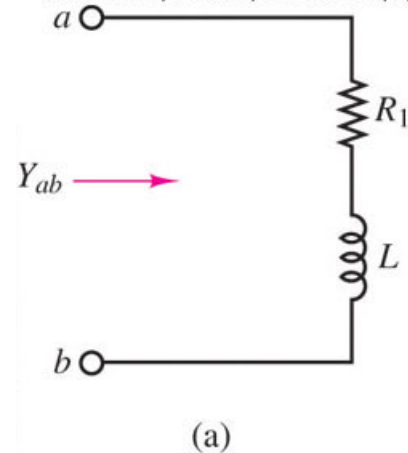Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Summary

- 1) Capacitors: Passes current at high frequency but blocks at DC
- 2) Inductor: Acts as short circuit at DC but blocks current at high frequency
- 3) Impedance introduced as a more general form to describe V/I (magnitude & phase)
- 4) Impedance depends on frequency
- 5) Represent these as phasors so we can add up impedances just like resistances in DC