

Nodal Voltage Analysis

Q1 [Alexander Problem 3.3]

Apply nodal voltage analysis to the circuit in Figure 3.52 to find v_o , I_1 , I_2 , I_3 , I_4 .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

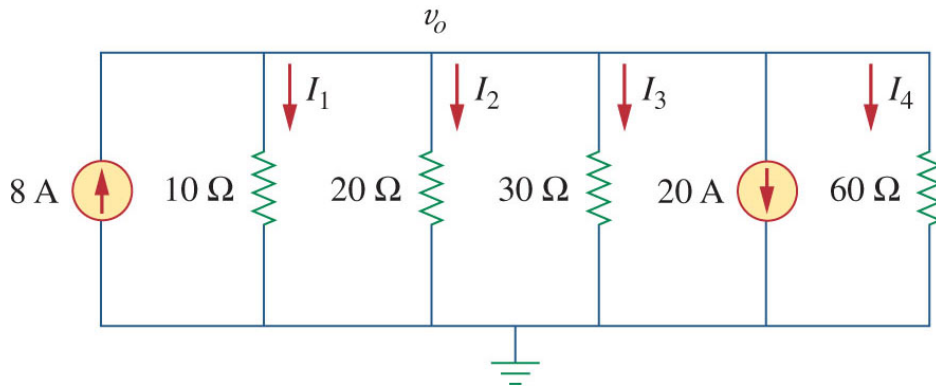


Figure 3.52

Q2 [Alexander Problem 3.5]

Apply nodal voltage analysis to the circuit in Figure 3.54 to find v_o .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

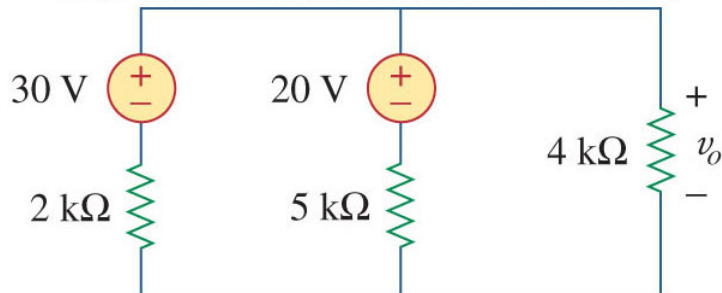


Figure 3.54

Q3 [Alexander Problem 3.11]

Apply nodal voltage analysis to the circuit in Figure 3.60 to find V_o and the power dissipated in all the resistors.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

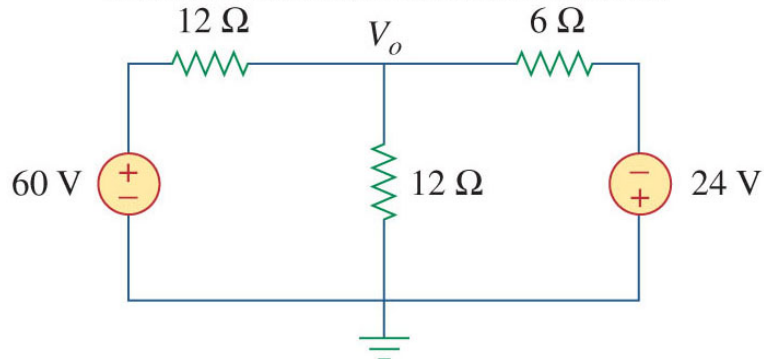


Figure 3.60

Q4 [Alexander Problem 3.32]

Find the nodal voltages v_1 , v_2 , v_3 in the circuit of Fig 3.81, and hence find all branch currents.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

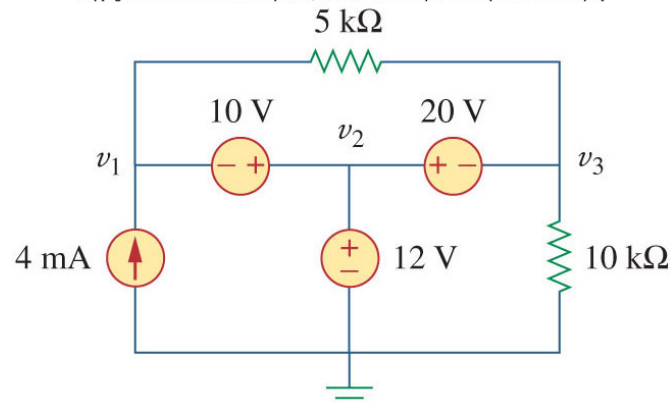


Fig 3.81

Q5 [Modified from Rizzoni Problem 3.12]

Find V_1 and V_2 in Figure P3.12 (relative to the node at the bottom of the circuit) using nodal voltage analysis. Then find V_L and use it to find the power delivered to the load resistor R_L .

Given: $R_1 = 8 \Omega$, $R_2 = 2 \Omega$, $R_3 = 5 \Omega$, $R_4 = 6 \Omega$, $R_L = 4 \Omega$, $V_S = 4 \text{ V}$, $I_S = 3 \text{ A}$.

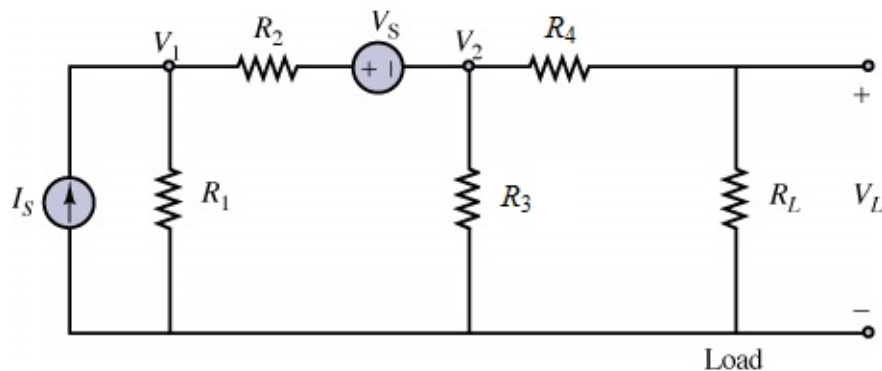


Figure P3.12

Q6 [Modified from Rizzoni Problem 3.62]

Apply nodal voltage analysis to the nodal voltage at A and B in Fig P3.5. Hence find the voltage across nodes A-B. Assume all resistors in the circuit are 100Ω and voltage sources are 5 V .

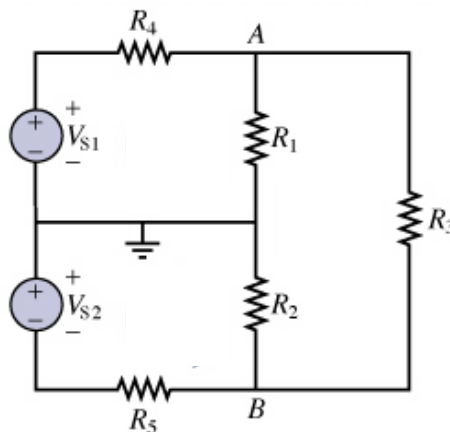


Figure P3.5

Mesh Current Analysis

Q7 [Modified from Alexander Problem 3.15]

Identify the number of mesh current equations needed to analyse the circuit in Figure 3.64. Then apply mesh current analysis to find i_o . Use i_o to find the nodal voltages V_1 , V_2 , V_3 .

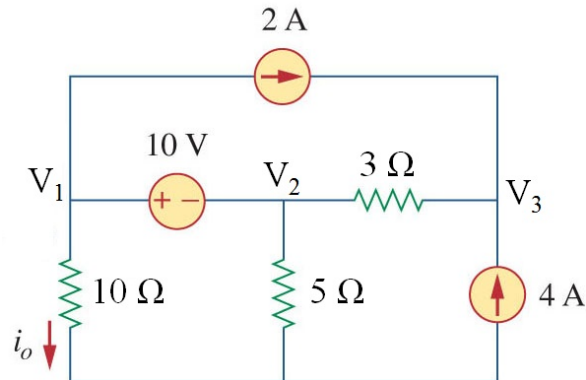


Figure 3.64

Q8 [Modified from Alexander Problem 3.36]

Identify the number of mesh current equations needed to analyse the circuit in Figure 3.84. Then apply mesh current analysis to find currents i_1 , i_2 , and i_3 .

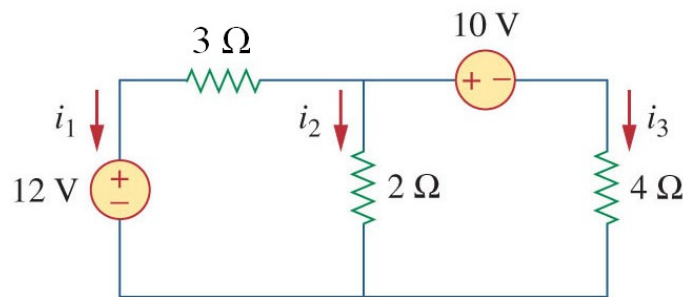


Figure 3.84

Q9 [Alexander Problem 3.51]

Identify the number of mesh current equations needed to analyse the circuit in Figure 3.96. Then apply mesh current analysis to find the voltage v_o .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

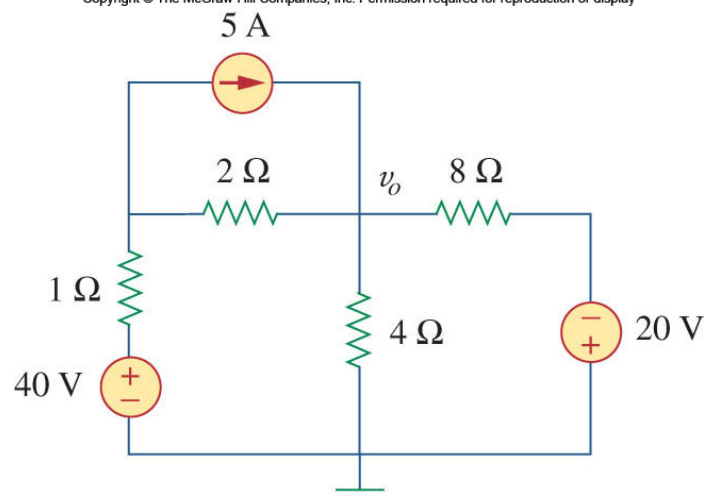


Figure 3.96

Numerical solutions**Q1 [Alexander Problem 3.3]**

$$v_o = -60 \text{ V}$$

$$I_1 = -6 \text{ A}, I_2 = -3 \text{ A}, I_3 = -2 \text{ A}, I_4 = -1 \text{ A}.$$

Q2 [Alexander Problem 3.5]

$$v_o = 20 \text{ V}$$

Q3 [Alexander Problem 3.11]

$$V_o = 3 \text{ V}$$

For the 12Ω resistor in series with the 60 V source: $P = 270.75 \text{ W}$

For the 12Ω resistor between V_o and ground: $P = 0.75 \text{ W}$

For the 6Ω resistor: $P = 121.5 \text{ W}$

Power generated by 60 V source = 285 W

Power generated by 24 V source = 108 W

Q4 [Alexander Problem 3.32]

$$v_1 = 2 \text{ V}, v_2 = 12 \text{ V}, v_3 = -8 \text{ V}$$

Q5 [Modified from Rizzoni Problem 3.12]

$$V_1 = 12 \text{ V}$$

$$V_2 = 5 \text{ V}$$

Power delivered to $R_L = 1 \text{ W}$

Q6 [Modified from Rizzoni Problem 3.62]

$$V_{AB} = 2.5 \text{ V}$$

Q7 [Modified from Alexander Problem 3.15]

Current through 10Ω : $i_o = 2 \text{ A}$

$$V_1 = 20 \text{ V}, V_2 = 10 \text{ V}, V_3 = 28 \text{ V}$$

Q8 [Modified from Alexander Problem 3.36]

$$i_1 = -2 \text{ A}; i_2 = 3 \text{ A}; i_3 = -1 \text{ A}$$

Q9 [Alexander Problem 3.51]

$$v_o = 20 \text{ V}$$