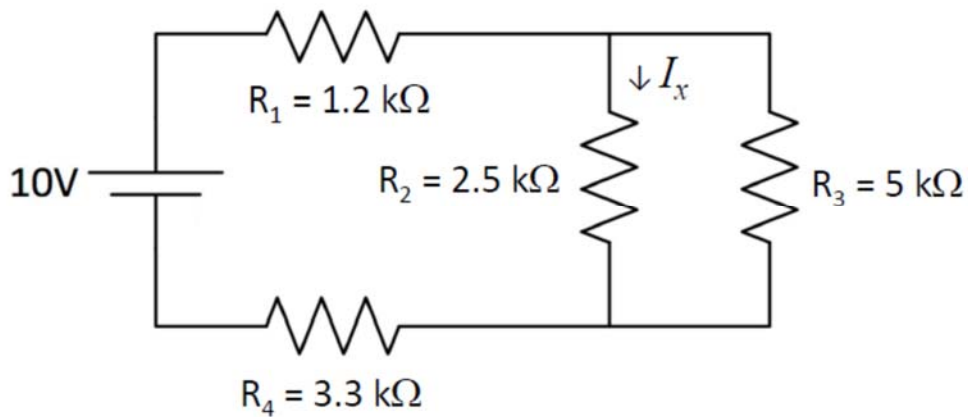


EE1002 Principle of Electronics

Assignment # 2

For each of the circuit diagrams given below, determine current value I_x as labelled.

(a)



(b)

